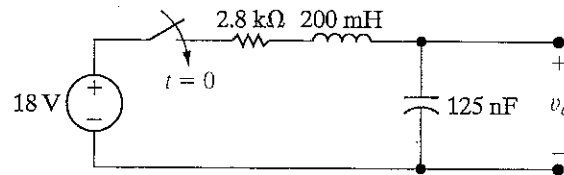


## HOMEWORK 4

- 13.15** Find  $V_o$  and  $v_o$  in the circuit shown in Fig. P13.15 if the initial energy is zero and the switch is closed at  $t = 0$ .

PSPICE  
MULTISIM


Figure P13.15



- 13.19** The switch in the circuit in Fig. P13.19 has been closed for a long time before opening at  $t = 0$ . Find  $v_o$  for  $t \geq 0$ .

PSPICE  
MULTISIM


Figure P13.19

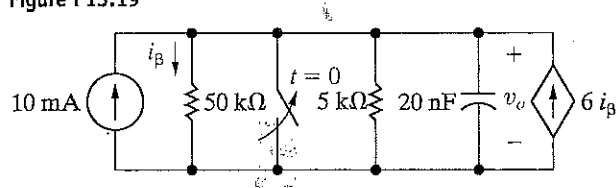

- 13.20** Find  $v_o$  in the circuit shown in Fig. P13.20 if  $i_g = 5u(t)$  mA. There is no energy stored in the circuit at  $t = 0$ .

PSPICE  
MULTISIM

Figure P13.20

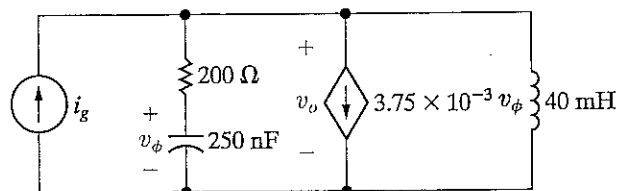


**13.27** There is no energy stored in the circuit in Fig. P13.27 at the time the current source is energized.

PSPICE  
MULTISIM

- Find  $I_a$  and  $I_b$ .
- Find  $i_a$  and  $i_b$ .
- Find  $V_a$ ,  $V_b$ , and  $V_c$ .
- Find  $v_a$ ,  $v_b$ , and  $v_c$ .
- Assume a capacitor will break down whenever its terminal voltage is 1000 V. How long after the current source turns on will one of the capacitors break down?

Figure P13.27

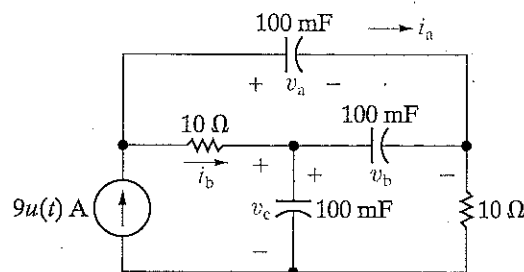

**13.28** There is no energy stored in the circuit in Fig. P13.28 at  $t = 0^-$ .

PSPICE  
MULTISIM

- Find  $V_o$ .
- Find  $v_o$ .
- Does your solution for  $v_o$  make sense in terms of known circuit behavior? Explain.

Figure P13.28

