


HOMEWORK 3

9.76 The sinusoidal voltage source in the circuit seen in Fig. P9.76 is operating at a frequency of 200 krad/s. The coefficient of coupling is adjusted until the peak amplitude of i_1 is maximum.

PSPICE
MULTISIM


- a) What is the value of k ?
- b) What is the peak amplitude of i_1 if $v_g = 560 \cos(2 \times 10^5 t)$ V?

Figure P9.76

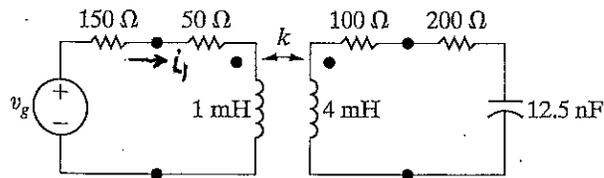


9.79 The value of k in the circuit in Fig. P9.79 is adjusted so that Z_{ab} is purely resistive when $\omega = 4$ krad/s. Find Z_{ab} .

Figure P9.79

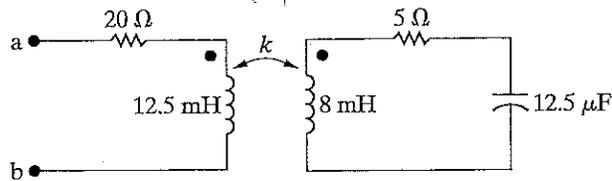


9.83 Find the impedance Z_{ab} in the circuit in Fig. P9.83 if $Z_L = 80 \angle 60^\circ \Omega$.

Figure P9.83

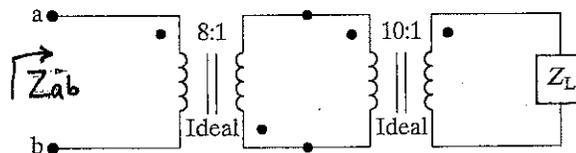

- 10.51** The values of the parameters in the circuit shown in Fig. P10.51 are $L_1 = 8 \text{ mH}$; $L_2 = 2 \text{ mH}$; $k = 0.75$; $R_g = 1 \Omega$; and $R_L = 7 \Omega$. If $v_g = 54\sqrt{2} \cos 1000t \text{ V}$, find
- the rms magnitude of v_o
 - the average power delivered to R_L
 - the percentage of the average power generated by the ideal voltage source that is delivered to R_L .

Figure P10.51

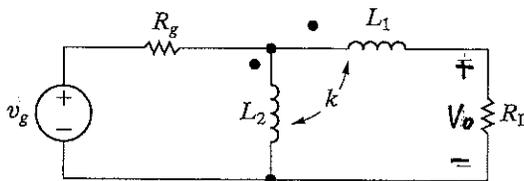

- 10.58** The sinusoidal voltage source in the circuit in Fig. P10.58 is operating at a frequency of 20 krad/s . The variable capacitive reactance in the circuit is adjusted until the average power delivered to the 100Ω resistor is as large as possible.
- Find the value of C in microfarads.
 - When C has the value found in (a), what is the average power delivered to the 100Ω resistor?
 - Replace the 100Ω resistor with a variable resistor R_o . Specify the value of R_o so that maximum average power is delivered to R_o .
 - What is the maximum average power that can be delivered to R_o ?

Figure P10.58

