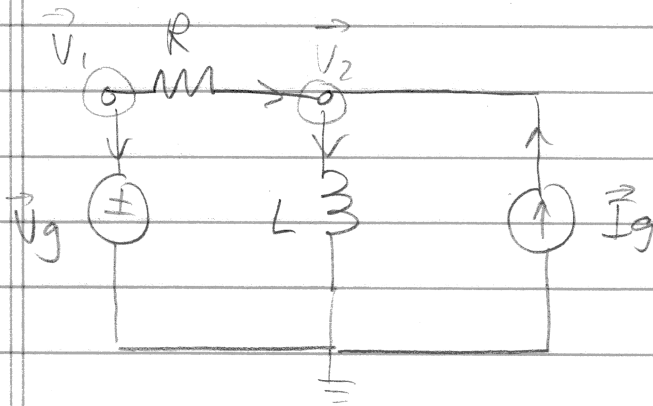


# The Node Voltage Method

①

## Example 1



$$R=1\Omega; L=1H$$

$$V_g=2\cos t \Rightarrow \vec{V}_g=2$$

$$i_g=5\cos t \Rightarrow \vec{I}_g=5$$

STEP 1

→ redrawn as phasor circuit

$$1) \vec{I}_{Vg} + \vec{I}_R = 0$$

$$\vec{I}_R = (\vec{V}_1 - \vec{V}_2)/R$$

$$\vec{I}_L = \vec{V}_2/j\omega L$$

$$\vec{I}_{Vg} = ?$$

$$2) -\vec{I}_R + \vec{I}_L - \vec{I}_g = 0$$

$$1) \vec{V}_1 = \vec{V}_g = 2$$

$$2) -\frac{(\vec{V}_1 - \vec{V}_2)}{R} + \frac{\vec{V}_2}{j\omega L} - 5 = 0$$

$$\Rightarrow 1) \vec{V}_1 = 2$$

$$2) -\frac{1}{R}\vec{V}_1 + \vec{V}_2\left(\frac{1}{R} + \frac{1}{j\omega L}\right) = 5$$

$1 + \frac{1}{j} = 1 - j$


$$\begin{bmatrix} 1 & 0 \\ -1 & 1-j \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 5 \end{bmatrix} \rightarrow \vec{V}_1 = 2$$

$$\vec{V}_2 = 3.5 + j3.5 = 4.95/45^\circ$$

$$V_1(t) = 2\cos t$$

$$V_2(t) = 4.95\cos(t+45^\circ)$$

(2)

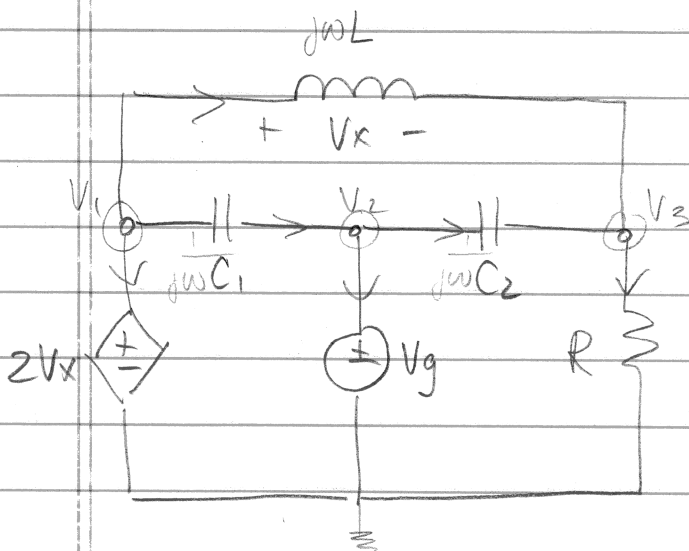Example 2 (Theremin)

$$R = 1 \Omega$$

$$C_1 = C_2 = 1 F$$

$$L = 1 H$$

$$V_g(t) = 5 \cos t$$

$\omega = 1 \text{ rad/s}$

$$1) \vec{I}_x + \vec{I}_L + \vec{I}_{C_1} = 0$$

$$2) -\vec{I}_{C_1} + \vec{I}_{V_g} + \vec{I}_{C_2} = 0$$

$$3) -\vec{I}_L - \vec{I}_{C_2} + \vec{I}_R = 0$$

$$\vec{I}_R = \vec{V}_3 / R$$

$$\vec{I}_L = (\vec{V}_1 - \vec{V}_3) / j\omega L$$

$$\vec{I}_{C_1} = j\omega C_1 (\vec{V}_1 - \vec{V}_2)$$

$$\vec{I}_{C_2} = j\omega C_2 (\vec{V}_2 - \vec{V}_3)$$

$$1) \vec{I}_{V_x} = ?$$

$$2) \vec{I}_{V_g} = ?$$

$$1) \vec{V}_1 = 2\vec{V}_x = 2(\vec{V}_1 - \vec{V}_3)$$

$$2) \vec{V}_2 = \vec{V}_g$$

$$3) -\frac{(\vec{V}_1 - \vec{V}_3)}{j\omega L} - j\omega C (\vec{V}_2 - \vec{V}_3) + \frac{\vec{V}_3}{R} = 0$$

$$1) \vec{V}_1 - 2\vec{V}_3 = 0$$

$$2) \vec{V}_2 = \vec{V}_g = 5$$

$$3) -\frac{1}{j\omega L} \vec{V}_1 - j\omega C \vec{V}_2 + \vec{V}_3 \left( \frac{1}{j\omega L} + j\omega C + \frac{1}{R} \right) = 0$$

$\frac{1}{j} = -j \quad \quad \quad -j = \frac{1}{j} \quad \quad \quad -j = \frac{1}{j} + j + 1$

(3)

$$\vec{V}_1 - 2\vec{V}_3 = 0$$



$$\vec{V}_2 = 5$$

$$j\vec{V}_1 - j\vec{V}_2 + \vec{V}_3 = 0$$


$$\begin{bmatrix} 1 & 0 & -2 \\ 0 & 1 & 0 \\ j & -j & 1 \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \\ \vec{V}_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 5 \\ 0 \end{bmatrix} \quad \begin{array}{l} \vec{V}_1 = 4 + j2 \\ \vec{V}_2 = 5 \\ \vec{V}_3 = 2 + j \end{array}$$

$$\Rightarrow \vec{V}_{th} = \vec{V}_3 = 2 + j$$

For  $Z_{th}$ :

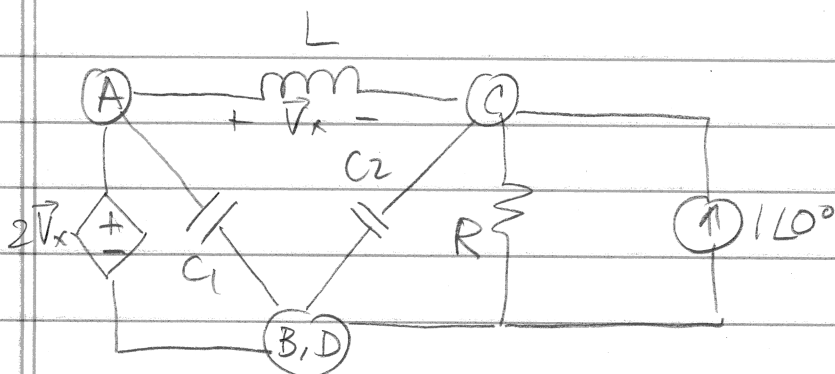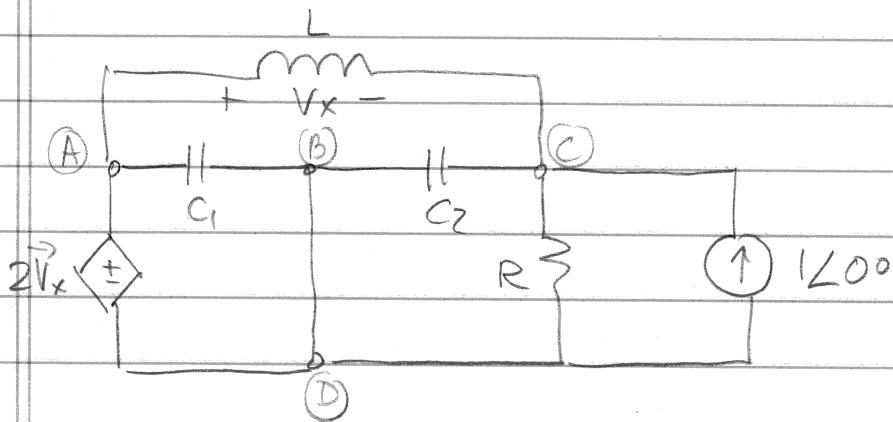

(4)

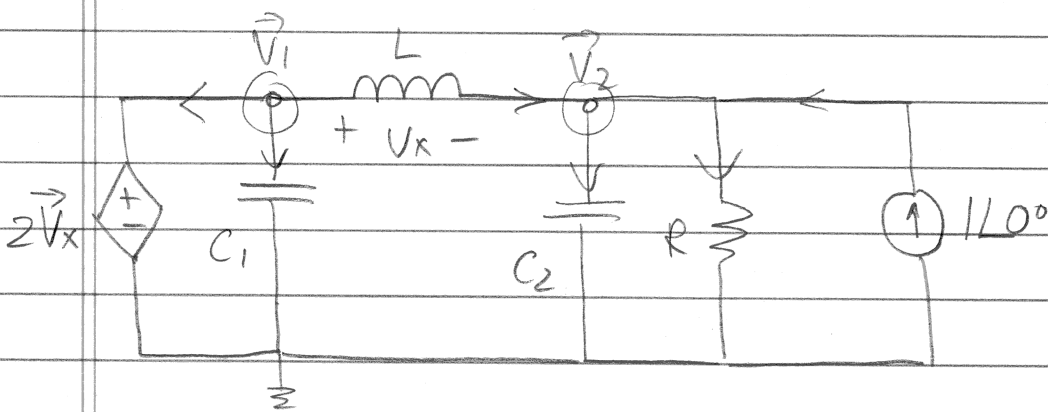

$$1) \vec{I}_{Vx} + \vec{I}_{C1} + \vec{I}_L = 0$$

$$2) -\vec{I}_L + \vec{I}_{C2} + \vec{I}_R - 1 = 0$$

$$1) \vec{V}_1 = 2\vec{V}_x = 2(\vec{V}_1 - \vec{V}_2)$$

$$2) -\frac{(\vec{V}_1 - \vec{V}_2)}{j\omega L} + j\omega C_2 \vec{V}_2 + \frac{\vec{V}_2}{R} = 1$$

$$\vec{I}_R = \vec{V}_2 / R$$

$$\vec{I}_L = (\vec{V}_1 - \vec{V}_2) / j\omega L$$

$$\vec{I}_{C1} = j\omega C_1 \vec{V}_1$$

$$\vec{I}_{C2} = j\omega C_2 \vec{V}_2$$

$$\vec{I}_{Vx} = ?$$

$$I_1$$

$$1) \vec{V}_1 - 2\vec{V}_2 = 0$$


$$2) -\frac{1}{j\omega L} \vec{V}_1 + \vec{V}_2 \left( \frac{1}{j\omega L} + j\omega C_2 + \frac{1}{R} \right) = 1$$

$\frac{1}{j} = -j$                        $\frac{1}{j} + j + 1$

$$\begin{bmatrix} 1 & -2 \\ j & 1 \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \Rightarrow \begin{aligned} \vec{V}_1 &= 0.4 - j0.8 \\ \vec{V}_2 &= 0.2 - j0.4 \end{aligned}$$

$$Z_{th} = \frac{\vec{V}_2}{1 \angle 0^\circ} = 0.2 - j0.4$$

### Example 3

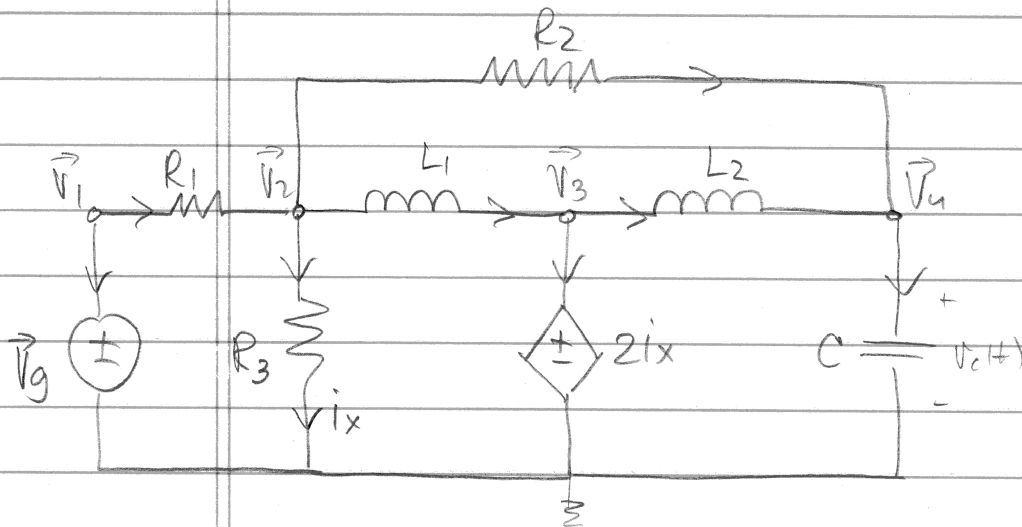

$$R_1 = R_2 = R_3 = 1 \Omega$$

$$L_1 = 1 \text{ H}$$

$$L_2 = 2 \text{ H}$$

$$C = \frac{1}{2} \text{ F}$$

$$V_g(t) = 10 \cos t$$

Find  $V_c(t)$

$$1) \quad \vec{I}_{V_g} + \vec{I}_{R_1} = 0$$

$$2) \quad -\vec{I}_{R_1} + \vec{I}_{R_3} + \vec{I}_{R_2} + \vec{I}_{L_1} = 0$$

$$3) \quad -\vec{I}_{L_1} + \vec{I}_{L_2} + \vec{I}_{2i_x} = 0$$

$$4) \quad -\vec{I}_{R_2} - \vec{I}_{L_2} + \vec{I}_C = 0$$

$$\vec{I}_{R_1} = (\vec{V}_1 - \vec{V}_2) / R_1$$

$$\vec{I}_{R_2} = (\vec{V}_2 - \vec{V}_4) / R_2$$

$$\vec{I}_{R_3} = \vec{V}_2 / R_3$$

$$\vec{I}_{L_1} = (\vec{V}_2 - \vec{V}_3) / j\omega L_1$$

$$\vec{I}_{L_2} = (\vec{V}_3 - \vec{V}_4) / j\omega L_2$$

$$\vec{I}_C = j\omega C \vec{V}_4$$

$$1) \quad \vec{V}_1 = \vec{V}_g = 10$$

$$I_1 \vec{I}_{V_g} = ?$$

$$I_2 \vec{I}_{2i_x} = ?$$

$$2) \quad -\frac{(\vec{V}_1 - \vec{V}_2)}{R_1} + \frac{\vec{V}_2}{R_3} + \frac{(\vec{V}_2 - \vec{V}_4)}{R_2} + \frac{(\vec{V}_2 - \vec{V}_3)}{j\omega L_1} = 0$$

$$3) \quad \vec{V}_3 = 2\vec{I}_x = 2\vec{I}_{R_3} = \frac{2\vec{V}_2}{R_3}$$

$$4) \quad -\frac{(\vec{V}_2 - \vec{V}_4)}{R_2} - \frac{(\vec{V}_3 - \vec{V}_4)}{j\omega L_2} + j\omega C \vec{V}_4 = 0$$

(6)

$$1) \vec{V}_1 = 10$$

$$2) -\frac{1}{R_1} \vec{V}_1 + \vec{V}_2 \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{j\omega L_1} \right) - \frac{1}{j\omega L_1} \vec{V}_3 - \frac{1}{R_2} \vec{V}_4 = 0$$

$\frac{1}{3} + \frac{1}{j} = 3 - j$

$$3) \frac{2}{R_3} \vec{V}_2 - \vec{V}_3 = 0$$

$$4) -\frac{1}{R_2} \vec{V}_2 - \frac{1}{j\omega L_2} \vec{V}_3 + \vec{V}_4 \left( \frac{1}{R_2} + \frac{1}{j\omega L_2} + j\omega C \right) = 0$$

$\frac{1}{j2} = -j/2$

$1 - j/2 + j/2$

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ -1 & 3-j & j & -1 \\ 0 & 2 & -1 & 0 \\ 0 & -1 & 0.5j & 1 \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \\ \vec{V}_3 \\ \vec{V}_4 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{aligned} \vec{V}_1 &= 10 \\ \vec{V}_2 &= 2.5 - j2.5 \\ \vec{V}_3 &= 5 - j5 \\ \vec{V}_4 &= -j5 \end{aligned}$$

$$\vec{V}_4 = -j5 = 5 \angle -90^\circ \Rightarrow v_4(t) = 5 \cos(t - 90^\circ) = 5 \sin t$$