

Power Calculations

①

Example 1


$$R_1 = R_2 = R_3 = R_4 = 1 \Omega$$

$$C_1 = C_2 = 1 F; L_1 = 2 H$$

$$L_2 = 1 H;$$

$$V_g(t) = 5 \sin t = 5 \cos(t - 90^\circ)$$

$$\vec{V}_g = 5 \angle -90^\circ = -j5$$

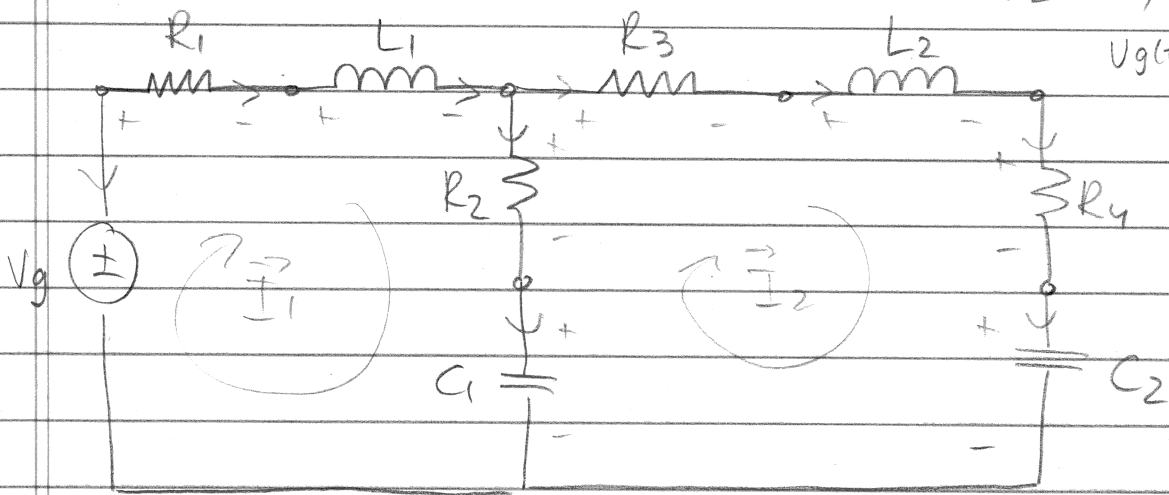

$$1) -\vec{V}_g + \vec{V}_{R1} + \vec{V}_{L1} + \vec{V}_{R2} + \vec{V}_{C1} = 0$$

$$\vec{V}_{R1} = R_1 \vec{I}_{R1} = R_1 \vec{I}_1$$

$$\vec{V}_{R2} = R_2 \vec{I}_{R2} = R_2 (\vec{I}_1 - \vec{I}_2)$$

$$2) \vec{V}_{R3} + \vec{V}_{L2} + \vec{V}_{R4} + \vec{V}_{C2} - \vec{V}_{C1} - \vec{V}_{R2} = 0$$

$$\vec{V}_{R3} = R_3 \vec{I}_{R3} = R_3 \vec{I}_2$$

$$\vec{V}_{R4} = R_4 \vec{I}_{R4} = R_4 \vec{I}_2$$

$$\vec{V}_{L1} = j\omega L_1 \vec{I}_{L1} = j\omega L_1 \vec{I}_1$$

$$\vec{V}_{L2} = j\omega L_2 \vec{I}_{L2} = j\omega L_2 \vec{I}_2$$

$$\vec{V}_{C1} = \frac{1}{j\omega C_1} \vec{I}_{C1} = \frac{1}{j\omega C_1} (\vec{I}_1 - \vec{I}_2)$$

$$\vec{V}_{C2} = \frac{1}{j\omega C_2} \vec{I}_{C2} = \frac{1}{j\omega C_2} \vec{I}_2$$

$$1) -\vec{V}_g + R_1 \vec{I}_1 + j\omega L_1 \vec{I}_1 + R_2 (\vec{I}_1 - \vec{I}_2) + \frac{1}{j\omega C_1} (\vec{I}_1 - \vec{I}_2) = 0$$

$$2) R_3 \vec{I}_2 + j\omega L_2 \vec{I}_2 + R_4 \vec{I}_2 + \frac{1}{j\omega C_2} \vec{I}_2 - \frac{1}{j\omega C_1} (\vec{I}_1 - \vec{I}_2) - R_2 (\vec{I}_1 - \vec{I}_2) = 0$$

$$1 + j2 + 1 + \frac{1}{j} = 2 + j \quad 1 + \frac{1}{j} = -j$$

$$1) \vec{I}_1 (R_1 + j\omega L_1 + R_2 + \frac{1}{j\omega C_1}) - \vec{I}_2 (R_2 + \frac{1}{j\omega C_1}) = \vec{V}_g = -j5$$

$$2) -\vec{I}_1 (R_2 + \frac{1}{j\omega C_1}) + \vec{I}_2 (R_3 + j\omega L_2 + R_4 + \frac{1}{j\omega C_2} + \frac{1}{j\omega C_1} + R_2) = 0$$

$$1 + \frac{1}{j} = -j \quad 1 + j + 1 + \frac{1}{j} + \frac{1}{j} + 1 = 3 - j$$

(2)

$$\begin{bmatrix} 2+j & -1+j \\ -1+j & 3-j \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} -j5 \\ 0 \end{bmatrix}$$

$$\vec{I}_1 = -1.3793 - j1.5517 \Rightarrow |\vec{I}_1| = 2.0761$$

$$\vec{I}_2 = -0.8621 - j0.3448 \Rightarrow |\vec{I}_2| = 0.9285$$

$$\vec{I}_{R2} = \vec{I}_{C1} = (\vec{I}_1 - \vec{I}_2) = -0.5172 - j1.2069 \Rightarrow |\vec{I}_{R2}| = |\vec{I}_{C1}| = 1.3131$$

$$S_{R1} = \frac{1}{2} |\vec{I}_{R1}|^2 \cdot Z_{R1} = \frac{1}{2} |\vec{I}_1|^2 \cdot 1 = \frac{1}{2} \cdot (2.0761)^2 \cdot 1 = 2.155 \text{ W}$$

$$S_{R2} = \frac{1}{2} |\vec{I}_{R2}|^2 \cdot Z_{R2} = \frac{1}{2} (1.3131)^2 \cdot 1 = 0.8621 \text{ W}$$

resistors
(active power
only)

$$S_{R3} = \frac{1}{2} |\vec{I}_{R3}|^2 \cdot Z_{R3} = \frac{1}{2} |\vec{I}_2|^2 \cdot 1 = \frac{1}{2} (0.9285)^2 \cdot 1 = 0.431 \text{ W}$$

$$S_{R4} = \frac{1}{2} |\vec{I}_{R4}|^2 \cdot Z_{R4} = \frac{1}{2} |\vec{I}_2|^2 \cdot 1 = 0.431 \text{ W}$$

capacitors

$$S_{C1} = \frac{1}{2} Z_{C1} \cdot |\vec{I}_{C1}|^2 = \frac{1}{2} \frac{1}{j\omega C_1} \cdot \underbrace{(1.3131)^2}_{1.7242} = -j \frac{1}{2} \cdot 1.7242 = -j0.8621$$

reactive
power
only


$$S_{C2} = \frac{1}{2} Z_{C2} \cdot |\vec{I}_{C2}|^2 = \frac{1}{2} \cdot \frac{1}{j\omega C_2} \cdot (0.9285)^2 = -j \frac{1}{2} \cdot 0.8621 = -j0.431$$

inductors

$$S_{L1} = \frac{1}{2} Z_{L1} \cdot |\vec{I}_{L1}|^2 = \frac{1}{2} \overset{j\omega}{(j\omega L_1)} \cdot (2.0761)^2 = j \cdot 4.31$$

$$S_{L2} = \frac{1}{2} Z_{L2} \cdot |\vec{I}_{L2}|^2 = \frac{1}{2} \overset{j}{(j\omega L_2)} \cdot (0.9285)^2 = j0.431$$

For the source:

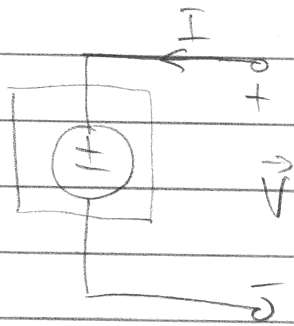

$$S = \frac{1}{2} \vec{V} \cdot \vec{I}^*$$

$$\vec{V} = \vec{V}_g = -j5 ; \quad \vec{I} = -\vec{I}_1 = 1.3793 + j1.5517$$

$$\Rightarrow S_g = \frac{1}{2} (-j5) \cdot (1.3793 - j1.5517) = -3.879 - j3.448$$

ACTIVE POWER DELIVERED $\Rightarrow 3.879 \text{ W}$ ✓ (source)

TOTAL ACTIVE POWER ABSORBED: (resistors)

$$2.155 + 0.8621 + 0.431 + 0.431 = 3.879 \text{ W} \quad \checkmark$$


REACTIVE POWER DELIVERED: (source + capacitors)

$$3.448 + 0.862 + 0.431 = 4.741 \text{ VAR} \quad \checkmark$$

REACTIVE POWER ABSORBED: (inductors)

$$4.31 + 0.431 = 4.741 \text{ VAR} \quad \checkmark$$

Example 2

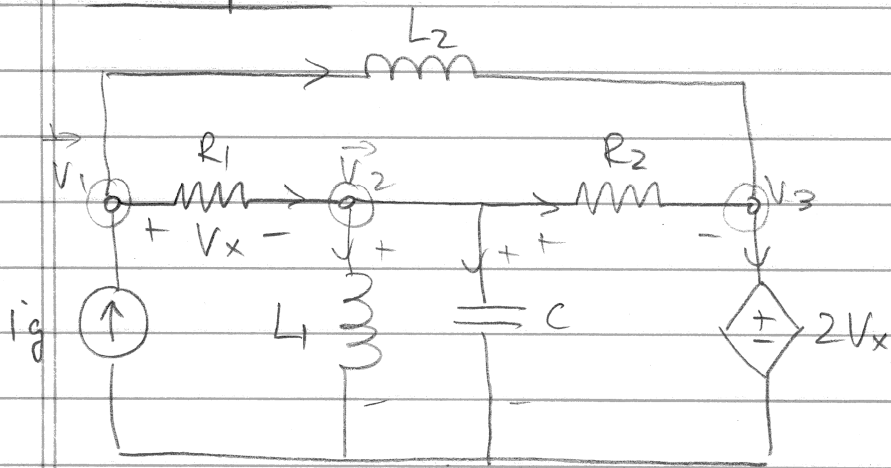

$$R_1 = R_2 = 1 \Omega$$

$$L_1 = L_2 = 1 \text{ H}$$

$$C = 4 \text{ F}$$

$$i_g(t) = \sin t = \cos(t - 90^\circ)$$

↓

$$\vec{I}_g = 1 \angle -90^\circ = -j$$

$$1) \quad -\vec{I}_g + \vec{I}_{R1} + \vec{I}_{L2} = 0$$

$$2) \quad -\vec{I}_{R1} + \vec{I}_{L1} + \vec{I}_C + \vec{I}_{R2} = 0$$

$$3) \quad -\vec{I}_{L2} - \vec{I}_{R2} + \vec{I}_X = 0$$

$$\vec{I}_{R1} = (\vec{V}_1 - \vec{V}_2) / R_1 = -1.4 - j0.2$$

$$\vec{I}_{R2} = (\vec{V}_2 - \vec{V}_3) / R_2 = 2.2 + j1.6$$

$$\vec{I}_{L1} = \vec{V}_2 / j\omega L_1 = 1.2 + j0.6$$

$$\vec{I}_{L2} = (\vec{V}_1 - \vec{V}_3) / j\omega L_2 = 1.4 - j0.8$$

$$\vec{I}_C = j\omega C \vec{V}_2 = -4.8 - j2.4$$

$$\vec{I}_X = ?$$

$$1) \quad -\vec{I}_g + \frac{(\vec{V}_1 - \vec{V}_2)}{R_1} + \frac{(\vec{V}_1 - \vec{V}_3)}{j\omega L_2}$$

$$2) \quad -\frac{(\vec{V}_1 - \vec{V}_2)}{R_1} + \frac{\vec{V}_2}{j\omega L_1} + j\omega C \vec{V}_2 + \frac{(\vec{V}_2 - \vec{V}_3)}{R_2} = 0$$

$$3) \quad \vec{V}_3 = 2\vec{V}_x = 2(\vec{V}_1 - \vec{V}_2)$$

$$1 + \frac{1}{j} = 1 - j \quad \quad \quad \frac{1}{j} = -j$$

$$1) \quad \vec{V}_1 \left(\frac{1}{R_1} + \frac{1}{j\omega L_2} \right) - \frac{1}{R_1} \vec{V}_2 - \frac{1}{j\omega L_2} \vec{V}_3 = \vec{I}_g = -j$$

$$1 + \frac{1}{j} + j4 + 1 = 2 + j3$$

$$2) \quad -\frac{1}{R_1} \vec{V}_1 + \vec{V}_2 \left(\frac{1}{R_1} + \frac{1}{j\omega L_1} + j\omega C + \frac{1}{R_2} \right) - \frac{1}{R_2} \vec{V}_3 = 0$$

$$3) \quad 2\vec{V}_1 - 2\vec{V}_2 - \vec{V}_3 = 0$$

$$\begin{bmatrix} 1-j & -1 & j \\ -1 & (2+j3) & -1 \\ 2 & -2 & -1 \end{bmatrix} \begin{bmatrix} \vec{V}_1 \\ \vec{V}_2 \\ \vec{V}_3 \end{bmatrix} = \begin{bmatrix} -j \\ 0 \\ 0 \end{bmatrix}$$

$$\vec{V}_1 = -2+j$$

$$\vec{V}_2 = -0.6+j1.2$$

$$\vec{V}_3 = -2.8-j0.4$$

resistors

$$S_{R1} = \frac{1}{2} Z_{R1} \cdot |\vec{I}_{R1}|^2 = \frac{1}{2} R_1 \cdot |-1.4-j0.2|^2 = 1.0 \text{ W}$$

$$S_{R2} = \frac{1}{2} Z_{R2} \cdot |\vec{I}_{R2}|^2 = \frac{1}{2} R_2 \cdot |2.2+j1.6|^2 = 3.7 \text{ W}$$


inductors

$$S_{L1} = \frac{1}{2} Z_{L1} \cdot |\vec{I}_{L1}|^2 = \frac{1}{2} j\omega L_1 \cdot |1.2+j0.6|^2 = 0.9j$$

$$S_{L2} = \frac{1}{2} Z_{L2} \cdot |\vec{I}_{L2}|^2 = \frac{1}{2} j\omega L_2 \cdot |1.4-j0.8|^2 = 1.3j$$

capacitor

$$S_C = \frac{1}{2} Z_C \cdot |\vec{I}_C|^2 = \frac{1}{2} \cdot \frac{1}{j\omega C} \cdot |-4.8-j2.4|^2 = -3.6j$$

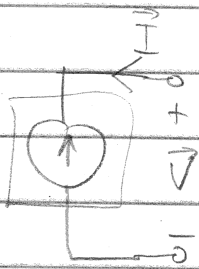


$$S_1 = \frac{1}{2} \vec{V} \cdot \vec{I}^*$$

$$\vec{V} = \vec{V}_1 = -2+j$$

$$\vec{I} = -\vec{I}_g = j$$

$$S_1 = \frac{1}{2} (-2+j)(-j) = 0.5+j$$

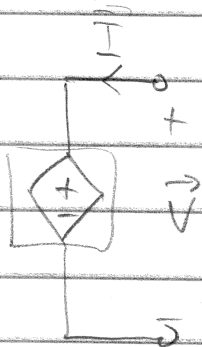

$$S_2 = \frac{1}{2} \vec{V} \cdot \vec{I}^*$$

$$\vec{V} = \vec{V}_3 = -2.8-j0.4$$

$$\vec{I} = \vec{I}_{R2} + \vec{I}_{L2} = 3.6+j0.8$$

$$S_2 = \frac{1}{2} (-2.8-j0.4)(3.6-j0.8) = -5.2+j0.4$$

(6)

ACTIVE POWER DELIVERED: 5.2 W ✓

← controlled source

ACTIVE POWER ABSORBED:

$$1 + 3.7 + 0.5 = 5.2 \text{ W} \checkmark$$

 $\begin{matrix} \uparrow & \uparrow & \uparrow \\ R_1 & R_2 & I_g \end{matrix}$

REACTIVE POWER DELIVERED:

$$3.6 \text{ VAR (capacitor)}$$

 $\begin{matrix} \uparrow \\ C \end{matrix}$

REACTIVE POWER ABSORBED:

$$0.9 + 1.3 + 1 + 0.4 = 3.6 \text{ VAR}$$

 $\begin{matrix} \uparrow & \uparrow & \uparrow & \uparrow \\ L_1 & L_2 & I_g & \text{ctrl. source} \end{matrix}$