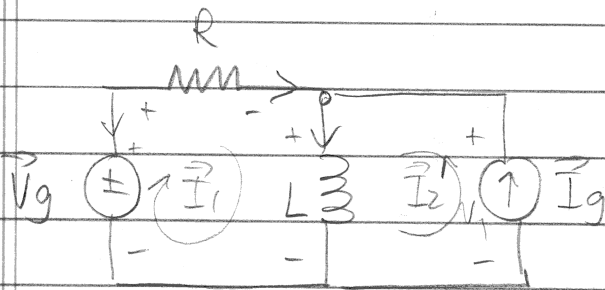


# The Loop Method

①

## Example 0



$$R = 1 \Omega ; L = 1 H$$

$$V_g = 2 \cos t \rightarrow \vec{V}_g = 2$$

$$I_g = 5 \cos t \rightarrow \vec{I}_g = 5$$

$$-\vec{V}_g + \vec{V}_R + \vec{V}_L = 0$$

$$\vec{V}_R = R \vec{I}_R = R \vec{I}_1$$

$$\vec{V}_L = j\omega L \vec{I}_L = j\omega L (\vec{I}_1 + \vec{I}_2)$$

$$-\vec{V}_g + \vec{V}_L = 0$$

$$\vec{V}_g = ?$$

$$-\vec{V}_g + R \vec{I}_1 + j\omega L (\vec{I}_1 + \vec{I}_2) = 0$$

R - exclusive to loop 1, dir +

L - shared by  $L_1$  &  $L_2$   
+ -

$$\vec{I}_2 = \vec{I}_g = 5$$

$$\vec{I}_1 (1 + j) + j \vec{I}_2 = 2$$

$$\vec{I}_2 = 5$$

$$\begin{bmatrix} 1+j & +j \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 5 \end{bmatrix}$$

$$\vec{I}_1 = -1.5 - j3.5$$


$$\vec{I}_2 = 5$$

$$\vec{I}_1 = 3.8079 \angle -113.2^\circ \rightarrow i_1(t) = 3.808 \cos(t - 113.2^\circ)$$

$$i_2(t) = 5 \cos t$$

# Example 1

①

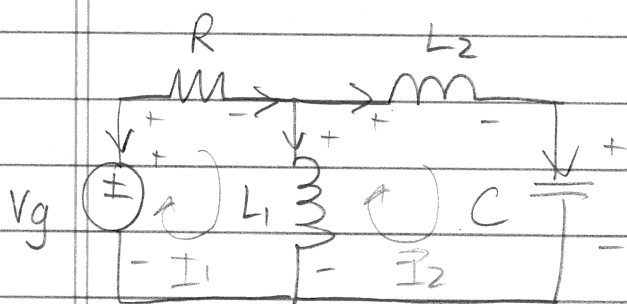

$$R = 1 \Omega$$

$$L_1 = L_2 = 1 \text{ H}$$

$$C = 2 \text{ F}$$

$$V_g(t) = 5 \cos t$$

$$-\vec{V}_g + \vec{V}_R + \vec{V}_{L_1} = 0$$

$$\vec{V}_R = R \vec{I}_R = R \vec{I}_1$$

$$\vec{V}_{L_1} = j\omega L_1 \vec{I}_{L_1} = j\omega L_1 (\vec{I}_1 - \vec{I}_2)$$

$$\vec{V}_{L_2} + \vec{V}_C - \vec{V}_{L_1} = 0$$

$$\vec{V}_{L_2} = j\omega L_2 \vec{I}_{L_2} = j\omega L_2 \vec{I}_2$$

$$\vec{V}_C = \frac{1}{j\omega C} \vec{I}_C = \frac{1}{j\omega C} \vec{I}_2$$

$$-\vec{V}_g + R \vec{I}_1 + j\omega L_1 (\vec{I}_1 - \vec{I}_2) = 0$$

$$j\omega L_2 \vec{I}_2 + \frac{1}{j\omega C} \vec{I}_2 - j\omega L_1 (\vec{I}_1 - \vec{I}_2) = 0$$

$$\Rightarrow \vec{I}_1 (1 + j) - j \vec{I}_2 = \vec{V}_g$$

$$-j \vec{I}_1 + \vec{I}_2 (1.5j) = 0$$


$$\begin{bmatrix} 1+j & -j \\ -j & 1.5j \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \end{bmatrix} \Rightarrow \begin{matrix} \vec{I}_1 = 4.5 - j1.5 \\ \vec{I}_2 = 3 - j \end{matrix}$$

$$\vec{I}_1 = 4.74 \angle -18.4^\circ \rightarrow i_1(t) = 4.74 \cos(t - 18.4^\circ)$$

$$\vec{I}_2 = 3.16 \angle -18.4^\circ \rightarrow i_2(t) = 3.16 \cos(t - 18.4^\circ)$$

## Example 2

(2)

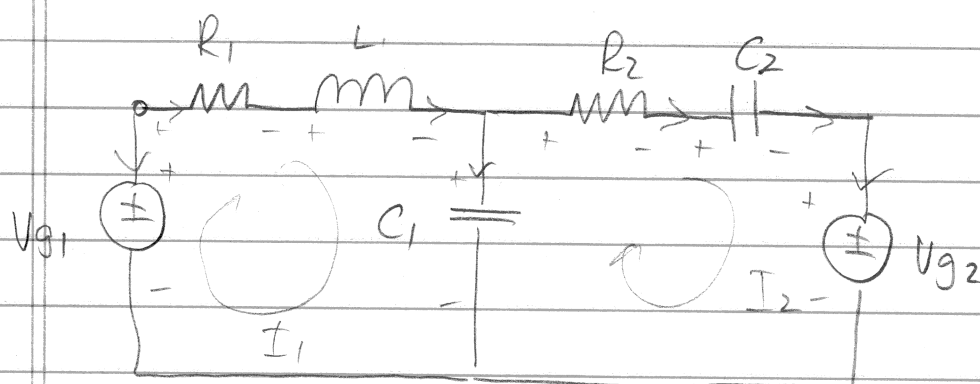

$$V_{g1} = 5 \cos 2t$$

$$V_{g2} = \cos 2t$$

$$R_1 = R_2 = 1 \Omega$$

$$L = 1H$$

$$C_1 = C_2 = 1F$$

$$-\vec{V}_{g1} + \vec{V}_{R1} + \vec{V}_L + \vec{V}_{C1} = 0$$

$$\vec{V}_{R1} = R_1 \vec{I}_{R1} = R_1 \vec{I}_1$$

$$\vec{V}_{R2} = R_2 \vec{I}_{R2} = R_2 \vec{I}_2$$

$$\vec{V}_L = j\omega L \vec{I}_L = j\omega L \vec{I}_1$$

$$\vec{V}_{C1} = \frac{1}{j\omega C_1} \vec{I}_{C1} = \frac{1}{j\omega C_1} (\vec{I}_1 - \vec{I}_2)$$

$$\vec{V}_{C2} = \frac{1}{j\omega C_2} \vec{I}_{C2} = \frac{1}{j\omega C_2} \vec{I}_2$$

$$\frac{1}{j} = -j$$

$$-\vec{V}_{g1} + R_1 \vec{I}_1 + j\omega L \vec{I}_1 + \frac{1}{j\omega C_1} (\vec{I}_1 - \vec{I}_2) = 0$$

$$R_2 \vec{I}_2 + \frac{1}{j\omega C_2} \vec{I}_2 + \vec{V}_{g2} - \frac{1}{j\omega C_1} (\vec{I}_1 - \vec{I}_2) = 0$$

$$\vec{I}_1 (1 + j2 - j\frac{1}{2}) - \frac{1}{j\omega C_1} \vec{I}_2 = \vec{V}_{g1} = 5$$

$$-\frac{1}{j\omega C_1} \vec{I}_1 + \vec{I}_2 (1 - j\frac{1}{2} - j\frac{1}{2}) = -\vec{V}_{g2} = -1$$

$$\begin{bmatrix} 1 + j1.5 & j0.5 \\ j0.5 & 1 - j \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 5 \\ -1 \end{bmatrix} \Rightarrow \vec{I}_1 = 1.472 - j1.904$$

$$\vec{I}_2 = -0.608 - j1.344$$


$$\vec{I}_1 = 2.4067 \angle -52.3^\circ$$

$$\rightarrow i_1(t) = 2.4067 \cos(2t - 52.3^\circ)$$

$$\vec{I}_2 = 1.4751 \angle -114.34^\circ$$

$$\rightarrow i_2(t) = 1.4751 \cos(2t - 114.34^\circ)$$

# Example 3

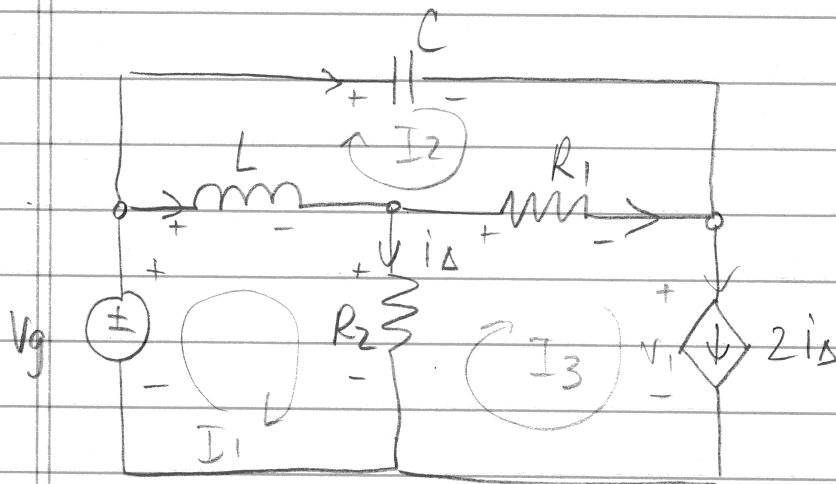

$$R_1 = R_2 = 1 \Omega$$

$$L = 0.5 H$$

$$C = 1 F$$

$$V_g(t) = 5 \sin 2t = 5 \cos(2t - 90^\circ)$$

$\omega = 2 \text{ rad/s}$

$$1) -\vec{V}_g + \vec{V}_L + \vec{V}_{R2} = 0$$

$$2) \vec{V}_C - \vec{V}_{R1} - \vec{V}_L = 0$$

$$3) \vec{V}_{R1} + \vec{V}_{2i\Delta} - \vec{V}_{R2} = 0$$

$$\vec{V}_{R1} = R_1 \vec{I}_{R1} = R_1 (\vec{I}_3 - \vec{I}_2)$$

$$\vec{V}_{R2} = R_2 \vec{I}_{R2} = R_2 (\vec{I}_1 - \vec{I}_3)$$

$$\vec{V}_L = j\omega L \vec{I}_L = j\omega L (\vec{I}_1 - \vec{I}_2)$$

$$\vec{V}_C = \frac{1}{j\omega C} \vec{I}_2$$

$$V_g \vec{V}_{2i\Delta} = ?$$

$$1) -\vec{V}_g + j\omega L (\vec{I}_1 - \vec{I}_2) + R_2 (\vec{I}_1 - \vec{I}_3) = 0$$

$$2) \frac{1}{j\omega C} \vec{I}_2 - R_1 (\vec{I}_3 - \vec{I}_2) - j\omega L (\vec{I}_1 - \vec{I}_2) = 0$$

$$3) \vec{I}_3 = 2 \vec{I}_\Delta = 2 (\vec{I}_1 - \vec{I}_3)$$

$$1) \vec{I}_1 (R_2 + j\omega L) - j\omega L \vec{I}_2 - R_2 \vec{I}_3 = \vec{V}_g = -j5$$

$$2) -j\omega L \vec{I}_1 + \vec{I}_2 (R_1 + \frac{1}{j\omega C} + j\omega L) - R_1 \vec{I}_3 = 0$$

$$3) 2\vec{I}_1 - 3\vec{I}_3 = 0$$

$$\begin{bmatrix} (1+j) & -j & -1 \\ -j & 1+0.5j & -1 \\ 2 & 0 & -3 \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \\ \vec{I}_3 \end{bmatrix} = \begin{bmatrix} -j5 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{aligned} \vec{I}_1 &= -0.4412 - j5.7353 \\ \vec{I}_2 &= 2.6471 - j5.5882 \\ \vec{I}_3 &= -0.2941 - j3.8235 \end{aligned}$$

$$\vec{I}_1 = 5.7522 \angle -94.39^\circ \quad \rightarrow \quad i_1(t) = 5.752 \cos(2t - 94.39^\circ)$$

$$\vec{I}_2 = 6.1835 \angle -64.65^\circ \quad \rightarrow \quad i_2(t) = 6.1835 \cos(2t - 64.65^\circ)$$

$$\vec{I}_3 = 3.8348 \angle -94.39^\circ \quad \rightarrow \quad i_3(t) = 3.8348 \cos(2t - 94.39^\circ)$$