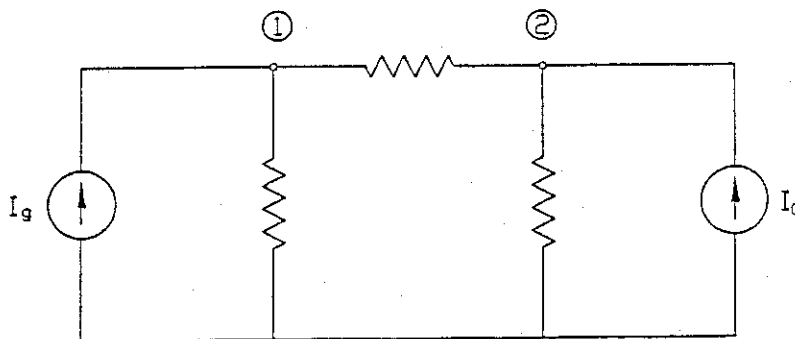


HOMEWORK # 4


PROBLEM 1. In the circuit below



all three resistors have a 1Ω resistance, and I_g is a constant current source with $I_g = 1\text{A}$. The other source, I_0 , is *nonlinear* and is defined by $I_0 = V_1^2$.

- a) Formulate the DC equations for this circuit using element stamps.
- b) Form the Jacobian for Newton's method.
- c) Solve the equations given the initial guess: $V_1(0) = V_2(0) = 0$.


PROBLEM 2. The circuit below

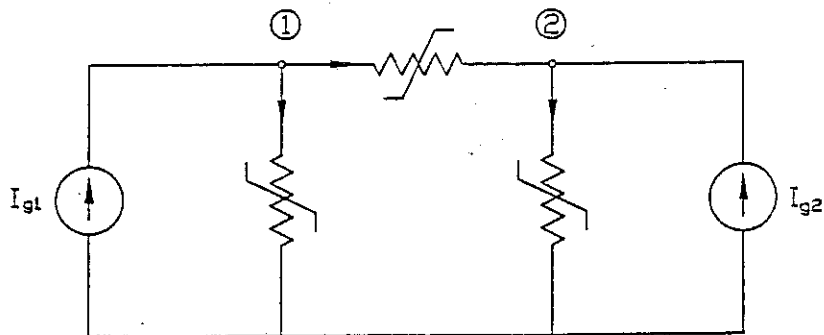

contains three *nonlinear* resistors, all of which are defined by $i = g(v) \equiv v^2$. Current sources I_{g1} and I_{g2} are constant, with $I_{g1} = 6\text{A}$ and $I_{g2} = 4\text{A}$.

- Formulate the DC equations for this circuit using element stamps.
- Form the Jacobian for Newton's method.
- Solve the equations given the initial guess: $V_1(0) = 0$ and $V_2(0) = 1$.
- Does it make sense to take $V_1(0) = 0$ and $V_2(0) = 0$ as the initial guess in this problem? Explain.

PROBLEM 3. In the circuit below

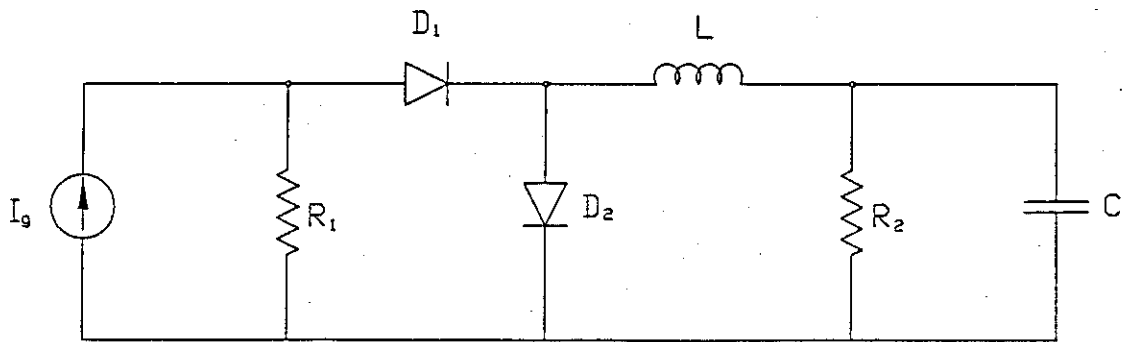

you are given: $R_1 = 1\text{K}$; $R_2 = 700\Omega$; $L = 10\text{ mH}$; $C = 1\mu\text{F}$ and $I_g = 1.5\text{ mA}$. The two diodes are identical, with $I_s = 10^{-14}\text{ A}$.

- Formulate the DC equations for this circuit using element stamps.
- Form the Jacobian for Newton's method.
- Determine a good initial guess for the voltages in this circuit. Explain your reasoning.
- Using the initial guess obtained in part c), compute the *exact* DC solution using Newton's method.

PROBLEM 4. Repeat parts c) and d) of Problem 3 using the following element values: $R_1 = 2\text{K}$; $R_2 = 2\text{K}$; $L = 10\text{ mH}$; $C = 1\mu\text{F}$; $I_g = 2\text{ mA}$ and $I_s = 10^{-14}\text{ A}$.