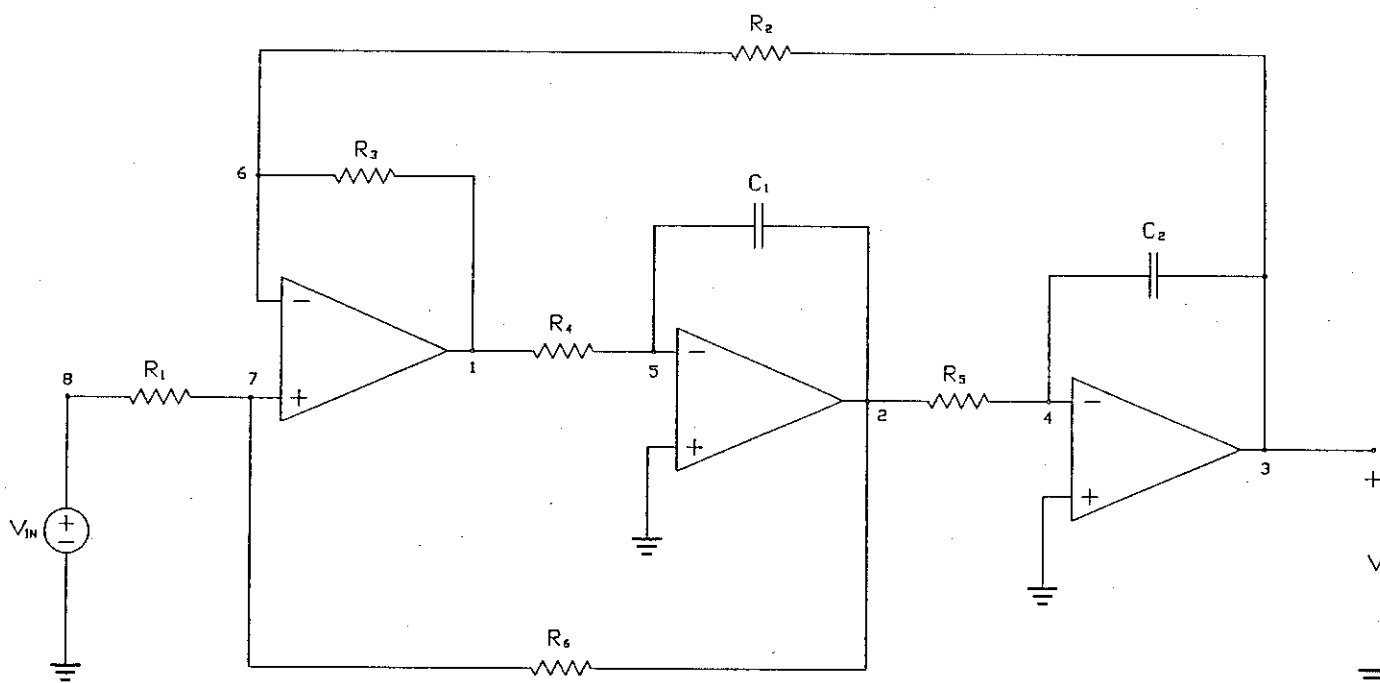


## PROJECT # 2: AC Simulation of Active Filters

The circuit below can be used to design *three* different types of filters; the specific filter characteristics will depend on whether the output voltage is taken from node 1, 2 or 3.



The element values in this circuit are:

$$R_1 = R_2 = R_3 = R_4 = R_5 = 1\text{K}; R_6 = 9\text{K}; C_1 = C_2 = 50\text{ }\mu\text{F}.$$

### PROBLEM 1.

Formulate the circuit equations for AC analysis. Indicate matrices  $G$ ,  $C$  and vector  $w$  explicitly.

## PROBLEM 2.

Create an m-file that will calculate the complex voltages in the circuit at different frequencies. The *input arguments* for this function should be matrices  $G$  and  $C$ , vector  $w$  and a vector  $z$  which consists of all the frequencies which are of interest. The *output arguments* should be the voltage magnitudes and phase angles at different frequencies. In other words your function should look something like: `[mag, phase] = bode1(G, C, w, z)`.

## PROBLEM 3.

- a) Use the function you created in Problem 2 to compute the magnitude and phase angle for voltages  $V_1$ ,  $V_2$  and  $V_3$ . Vector  $z$  should contain frequencies ranging from 0.1 Hz to 1kHz (ten points per decade should suffice).
- b) Obtain separate plots for the *magnitudes* of voltages  $V_1$ ,  $V_2$  and  $V_3$ . The voltage magnitudes should be in *decibels*, and a semilog scale should be used (function `semilogx(z, A)` in Matlab).
- c) Based on the plots obtained in part b), determine what types of filters are realized when the output voltage is taken from nodes 1, 2 and 3, respectively.
- d) Obtain separate plots for the *phase angles* of voltages  $V_1$ ,  $V_2$  and  $V_3$ . As in part b), use a semilog scale, and display the phase angles in *radians*.

## PROBLEM 4.

- a) Perform an AC analysis of this circuit in SPICE. Print out your *input file*.
- b) Obtain separate *magnitude plots* for voltages  $V_1$ ,  $V_2$  and  $V_3$  in SPICE.
- c) Obtain separate *phase plots* for voltages  $V_1$ ,  $V_2$  and  $V_3$  in SPICE.
- d) Compare the results of your program with those of SPICE.